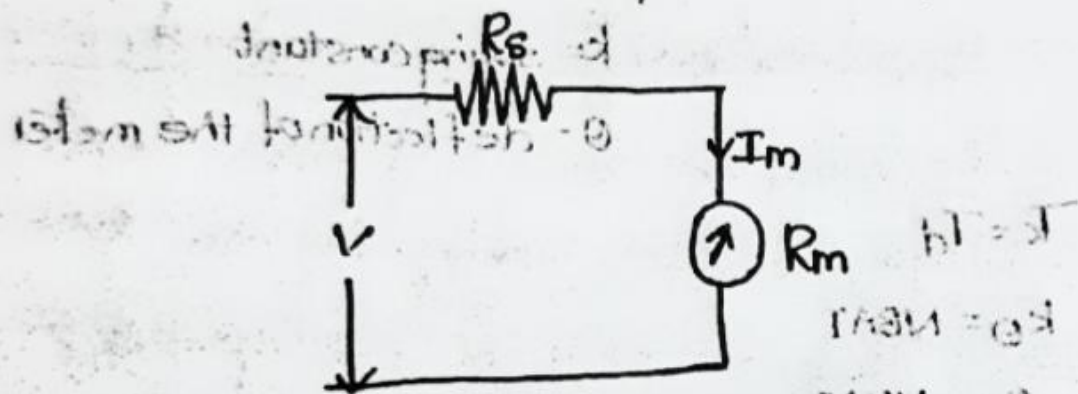


Basic Dc Voltmeter:



→ A Dc Voltmeter is use to measure the potential difference between 2 point in a dc Circuit (or) ckt Component

→ The basic DArsonval movement is converted into Voltmeter by using a Series resistor called as Multiplier

→ The function of multipliers is to limit the current through the Basic meter then the current doesn't exceed full scale deflection current

→ To Measure the potential difference b/w two points in a DC ckt. the Voltmeter is always connected across them with proper polarity.

$$V = I_m (R_s + R_m)$$

$$R_s + R_m = \frac{V}{I_m}$$

$$R_s = \frac{V}{I_m} - R_m$$


Where $I_m = I_{fSD}$ = full scale deflection of the current

R_m = internal resistance of a coil

R_s = Series resistance (or) Multiplier resistance
(or) Current limiting resistance

V = full range voltage of the instrument

Multirange Voltmeter :-

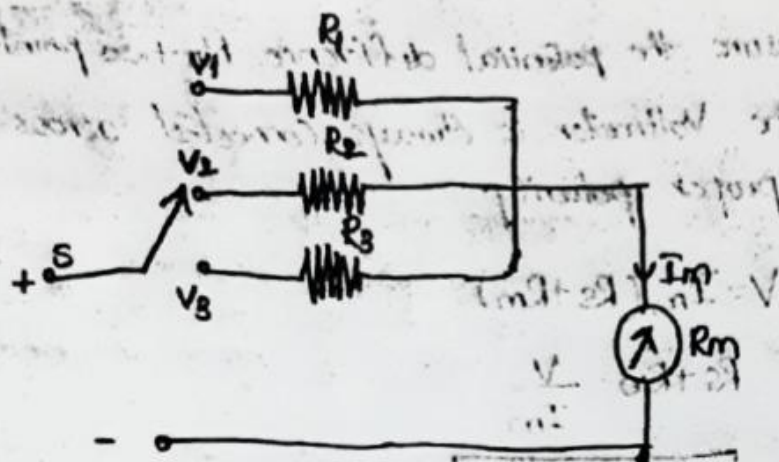

→ The DC voltmeter is converted into multirange voltmeter by using number of multipliers and a selector switch as shown in fig.

→ Let \$R_1, R_2, R_3\$ are multipliers that gives voltage ranges \$V_1, V_2, V_3\$

→ The Multiposition switch is used to select the multiplier for required voltage range.

for \$V_1 > V_2 > V_3\$ then the multipliers \$R_1 > R_2 > R_3\$ and the multiplier resistors are given by \$V_1 = I_m(R_1 + R_m)\$

$$R_1 = \frac{V_1}{I_m} - R_m$$

$$\text{Similarly } R_2 = \frac{V_2}{I_m} - R_m$$

$$R_3 = \frac{V_3}{I_m} - R_m$$

→ These Voltmeter requires high precision values of multiple resistance, which increases the cost.

