

A very important bridge used for the precision measurement of capacitors and their insulating properties is the Schering bridge. Its basic circuit arrangement is given in Fig. 11.26. The standard capacitor  $C_3$  is a high quality mica capacitor (low-loss) for general measurements, or an air capacitor (having a very stable value and a very small electric field) for insulation measurement.

For balance, the general equation is

$$Z_1 Z_x = Z_2 Z_3$$

$$\therefore Z_x = \frac{Z_2 Z_3}{Z_1}, Z_x = Z_2 Z_3 Y_1$$

where

$$Z_x = R_x - j/\omega C_x$$

$$Z_2 = R_2$$

$$Z_3 = -j/\omega C_3$$

$$Y_1 = 1/R_1 + j \omega C_1$$

as

$$Z_x = Z_2 Z_3 Y_1$$

$$\therefore \left( R_x - \frac{j}{\omega C_x} \right) = R_2 \left( \frac{-j}{\omega C_3} \right) \times \left( \frac{1}{R_1} + j \omega C_1 \right)$$

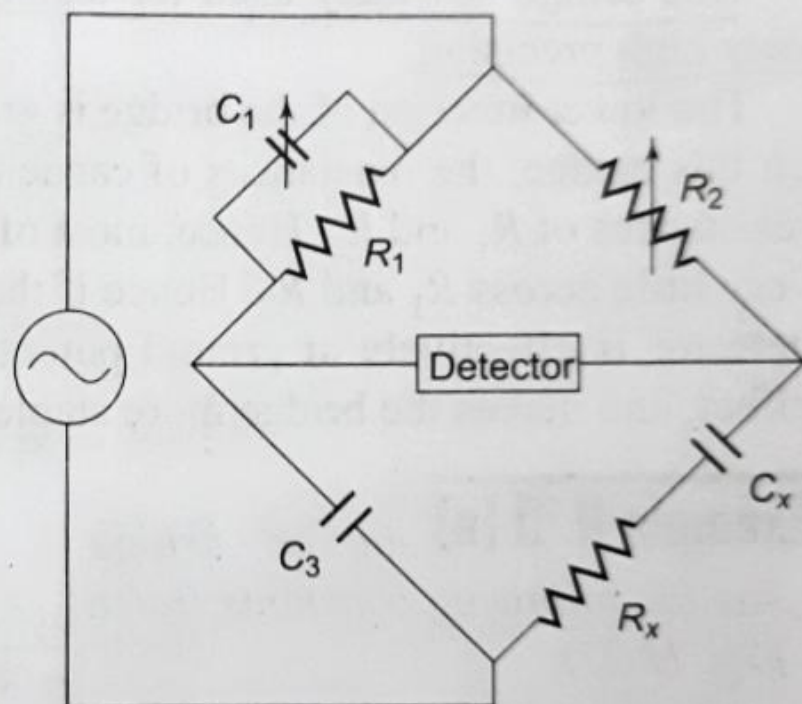


Fig. 11.26 Schering's bridge

$$\left( R_x - \frac{j}{\omega C_x} \right) = \frac{R_2 (-j)}{R_1 (\omega C_3)} + \frac{R_2 C_1}{C_3}$$

Equating the real and imaginary terms, we get

$$R_x = \frac{R_2 C_1}{C_3} \quad [11.20(a)]$$

and  $C_x = \frac{R_1}{R_2} C_3 \quad [11.20(b)]$

The dial of capacitor  $C_1$  can be calibrated directly to give the dissipation factor at a particular frequency.

The dissipation factor  $D$  of a series RC circuit is defined as the cotangent of the phase angle.

$$\checkmark D = \frac{R_x}{X_x} = \omega C_x R_x$$

Also,  $D$  is the reciprocal of the quality factor  $Q$ , i.e.  $D = 1/Q$ .  $D$  indicates the quality of the capacitor.