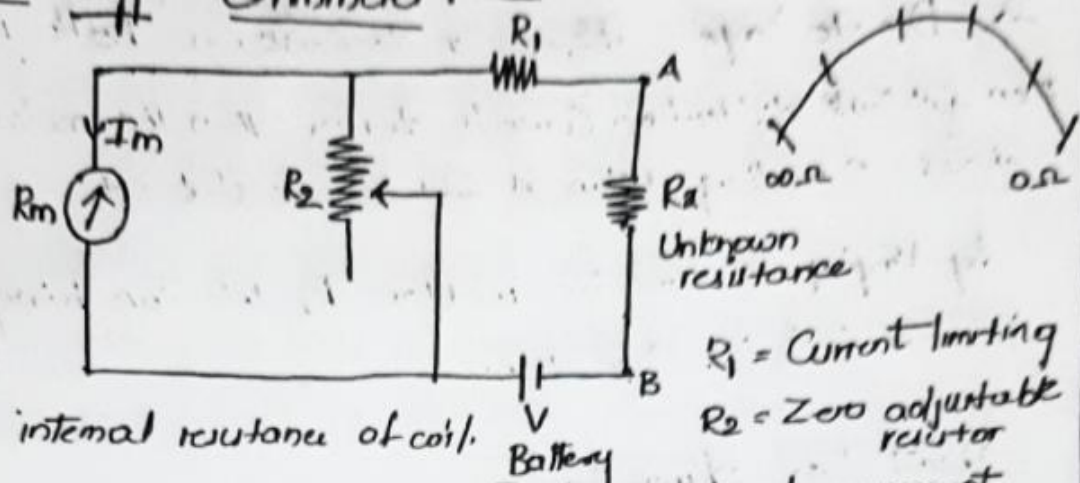


# Series Type Ohmmeter :-



$R_m$  = internal resistance of coil.

→ The Series type ohmmeter consists of Universal movement connected in series with multiplier resistance ' $R_1$ ' and the battery ' $V$ '.

→ The Unknown resistance ' $R_x$ ' is connected in series with the basic meter as shown in fig.

→ The deflection of the meter depends on the magnitude of Unknown resistance ' $R_x$ '.

The calibration of series type of ohmmeter is as follows

i)  $R_x = 0$  (A+B short ckt)

ii) Max Current flows through the meter.

iii) The resistor  $R_2$  is adjusted to get the full scale deflection current through the meter.

Then the position of pointer is marked as One on the scale.

ii)  $R_2 = \infty$  (A+B are open ckt)

The current flows through the meter is Zero hence the position of pointer is marked as  $\infty \Omega$  on the scale.

iii) Half scale position resistance ( $R_h$ ):-

It is the value of  $R_x$  at which the meter gives half of the full scale deflection current.

$$R_h = (R_m \parallel R_2) + R_1$$

$$R_1 + \left( \frac{R_m R_2}{R_m + R_2} \right)$$


→ The intermediate readings can be found by using non value of  $R_x$ .

→ Since Current is inversely proportional to resistance and meter reading is  $\infty$  to 0.2

→ Due to age, there is a decrease in battery voltage then full scale deflection current draws then the meter doesn't show 0 reading when A and B are short ckt.

by Varying the Variable resistor  $R_2$  We can bring the pointer back to 0 position.

### Shunt type ohmmeter:

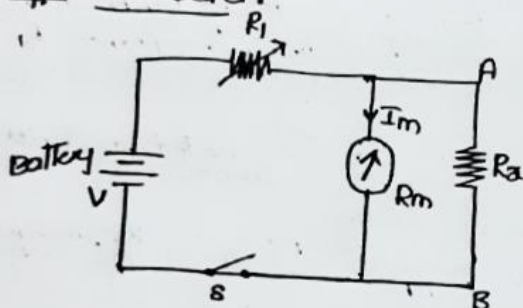

→ The shunt type ohmmeter consists of a d'Arsonval movement connected in series with multiplier resistance and battery.

→ The unknown resistor  $R_x$  is connected across the basic meter as shown in fig.

→ The current flows through the meter the magnitude of unknown resistance.

→ The switch S is provided to remove the battery when the instrument is not used.

→ The calibration of shunt type ohmmeter is as follows

(i) on known resistance:  $R_x = 0$  (A & B short ckt)

No. Current flows the meter then the pointer position is marked as '0' volts on the scale (ii)  $R_x = \infty$  (A & B open ckt)



→ The entire current flows through the meter by varying resistor  $R_1$  to get the full scale deflection current of the meter. Then the pointer position marked as  $\infty$ .

iii) Half scale position resistance  $R_h$

→ It is the value of  $R_x$  at which the current through the meter is half of the full scale deflection current of the meter.

→ The intermediate markings are made by connecting different known values.

→ Due to time and age there is a decreasing battery voltage. due to this full scale deflection current decreases. hence the meter doesn't show full scale reading. When the terminals A and B are opened.

→ Then by varying the resistor  $R_1$  it is possible to bring the pointer back to full scale deflection current of the meter.

→ The shunt type ohmmeter has used to measure low resistance value. AC Voltages